



FACULTY OF ENGINEERING

CAIRO UNIVERSITY


LAB 1

INTRODUCTION TO VHDL

CMPN301: COMPUTER ARCHITECTURE COURSE

EXERTED FROM DR. ADNAN SHAOUT- *THE UNIVERSITY OF MICHIGAN-DEARBORN*

DESIGN FLOW

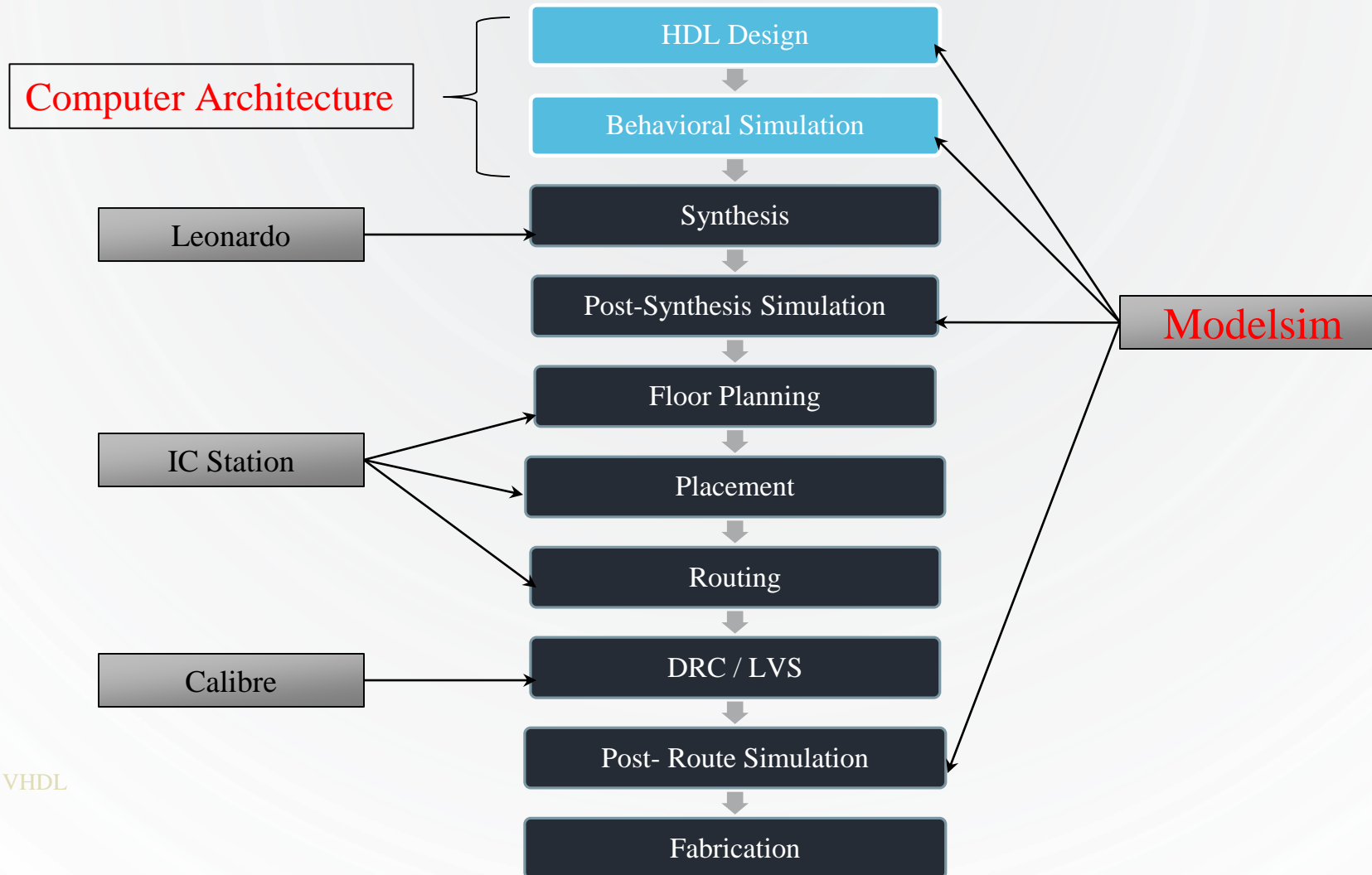



OBJECTIVES

- Define VHDL and its usage
- Understand different modeling techniques in designing digital circuits (Dataflow , structural)
- Understand the Hardware created from the VHDL code
- Understand Concurrent statement
- Reuse previously created entity (component instantiation a.k.a port mapping)
- Practice designing with VHDL



WHAT IS VHDL?

- VHSIC Hardware Description Language
- VHDL is a programming language that allows one to model and develop complex digital systems.



WHY VHDL?

- Requirements specification
- Documentation
- Testing using simulation
- Formal verification
- Synthesis
- Class assignments 😊



HW DESIGNER GOAL

- Most ‘reliable’ design process, with minimum cost and time.
- Avoid design errors!

The slide features decorative circuit board patterns in the corners, consisting of black lines and small circles representing components or vias. The background has a light gray circular gradient.



*VHDL is **Describing Hardware** so every line counts
and cost a lot in real world*

VHDL LANGUAGE: VARIABLES


- Variables are Wires
- Assignment are “<=” or “:=” instead of “=”

$X \leq C \text{ and } D;$

$W \leq E \text{ nor } F;$

  

VHDL LANGUAGE: MODEL DEFINITION

 

Images are from <http://vlsiuniverse.blogspot.com.eg/2016/07/multiplexer.html>

-
- A decorative graphic consisting of several vertical and diagonal lines of varying lengths, some ending in small circles, resembling a stylized circuit board or a network diagram. The lines are black and the circles are white with black outlines.


```
ENTITY mux2 IS  
    PORT ( IN1,IN2,SEI: IN std_logic;  
           OUT1      : OUT std_logic);  
END ENTITY mux2;
```

VHDL LANGUAGE: MODEL IMPLEMENTATION


ARCHITECTURE arch1 **OF** mux2 **IS**
BEGIN

out1 <= (in1 and (not Sel))
or
(in2 and Sel);

END arch1;

 

LET'S MAKE A MUX 4X1

 

MUX 4X1

ENTITY *mux4* ***IS***


PORT(*in0,in1,in2,in3: IN std_logic;*

sel : IN std_logic_vector (1 DOWNT0 0);

out1: OUT std_logic);

END *mux4;*

INTRO TO VHDL

 

A decorative graphic consisting of black lines and circles, resembling a circuit board or a stylized tree, is positioned on the left side of the slide. The lines branch out from the top and bottom, with small circles at the ends of some branches.

VHDL LANGUAGE: MODEL IMPLEMENTATION

- MODEL Implementation is called Architecture
- Types of Modeling:
 - Dataflow
 - Describes the flow of data within a component/system.
 - Structural
 - Describes the component by the interconnection of lower level components/primitives
 - Behavioral (next time)
 - Describes the functionality of a component/system usually using a process
 - Mixed of the above ways

VHDL LANGUAGE: MODEL IMPLEMENTATION


DATA FLOW

ARCHITECTURE arch1 **OF** mux4 **IS**
BEGIN

```
out1 <= in0 WHEN sel(0) = '0' AND sel(1) = '0'  
      ELSE in1 WHEN sel(0) = '0' AND sel(1) = '1'  
      ELSE in2 WHEN sel(0) = '1' AND sel(1) = '0'  
      ELSE in3;
```

END arch1;

INTRO TO VHDL

 




VHDL LANGUAGE: MODEL IMPLEMENTATION

STRUCTURAL

- Can we Make Mux 4x1 from Mux 2x1 ?

VHDL LANGUAGE: MODEL IMPLEMENTATION

STRUCTURAL

 

VHDL LANGUAGE: MODEL IMPLEMENTATION

STRUCTURAL

When we use another entity inside our architecture we call it component

ARCHITECTURE struct **OF** mux4 **IS**

COMPONENT mux2 **IS**

PORT (IN1,IN2,SEL: **IN** std_logic;
OUT1 : **OUT** std_logic);

END COMPONENT ;


Signal are considered as wires

SIGNAL x1,x2 : std_logic;

Begin

Signal type

Notice there is no direction for signals

 

VHDL LANGUAGE: MODEL IMPLEMENTATION

STRUCTURAL

When we use another entity inside our architecture we call it component

ARCHITECTURE struct **OF** mux4 **IS**

COMPONENT mux2 **IS**

PORT (IN1,IN2,SEL: **IN** std_logic;
OUT1 : **OUT** std_logic);

END COMPONENT ;

Signal are considered as wires

SIGNAL x1,x2 : std_logic;

Begin

Signal type
Notice there is no direction for signals

- *Till here we told our circuit that there is a component called mux2 and this is how to connect to it but we didn't use it yet*

VHDL LANGUAGE: MODEL IMPLEMENTATION

STRUCTURAL (CONT)

BEGIN

Keyword, whenever I port map a component I put it in the circuit (as hardware IC)

u0: mux2 PORT MAP (in0,in1,s(0),x1);

u1: mux2 PORT MAP (in2,in3,s(0),x2);

u2: mux2 PORT MAP (x1,x2,s(1),out1);


END struct;

Label to identify component with while tracing

Component name

Parameters sent to the component in the same order they are mentioned in the declaration

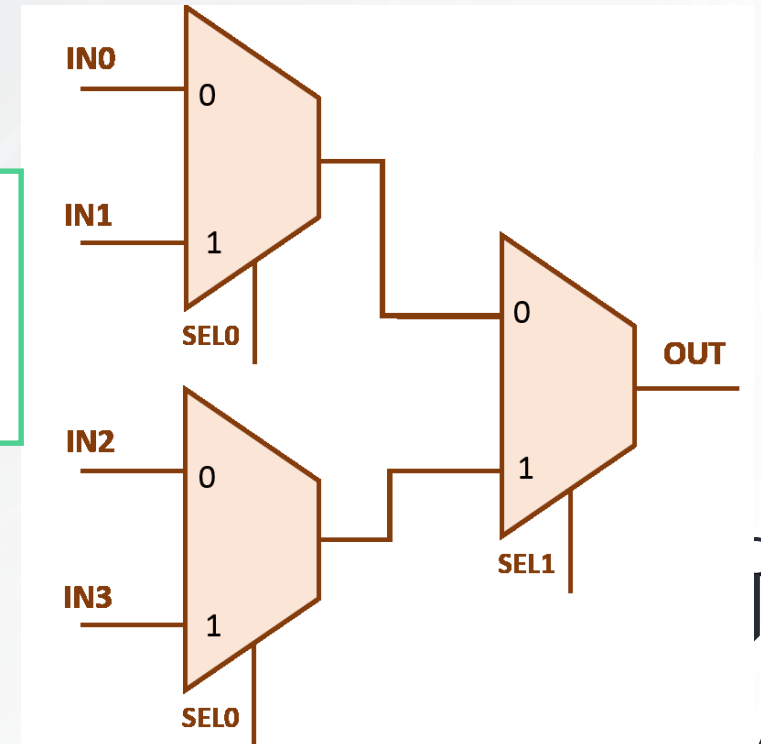Concurrent statements
All executes at the same time



VHDL LANGUAGE: MODEL IMPLEMENTATION

STRUCTURAL (CONT)


BEGIN

u0: mux2 PORT MAP (in0,in1,s(0),x1);

u1: mux2 PORT MAP (in2,in3,s(0),x2);

u2: mux2 PORT MAP (x1,x2,s(1),out1);

END struct;

 

DATA TYPE (STD_LOGIC)

- Include
 - Library ieee;
 - Use ieee.std_logic_1164.all
- Std_logic Possible values
 - 1 or 0
 - X → for conflict
 - Z → high impedance (remember tristate buffer?)
 - U → undefined
 - others
- Think: What do you think possible values of Data Type (bit) ?
- Which is better to use bit or std_logic?

DATA TYPE (STD_LOGIC_VECTOR)

- Std_logic_vector
 - **a,b : in std_logic_vector(2 downto 0)**
 - Can be accessed like b(2) , b(1)
- To access all vector
 - a <= b;
- To access a range of the vector
 - b(1 downto 0) <= a(2 downto 1)
- ‘&’ operator to concatenate two vectors or vector and single element
 - b(1 downto 0) <= a(2) & ‘0’

Still confused !!

- Consider the module as a function or class
- The entity declaration is like a header for the function (interface to our module)
- The architecture is the implementation of the function (how this module behaves inside)
- Whenever I want to use function in another , I have to include that function header (that's when I introduce the module between architecture and begin)
- The actual usage of the function happens when we call it – function call- this is like port mapping a component But ...

Important Consideration

- Whenever you use port map , **you add a component to the circuit** , it is not like a function that you can call it and re-call it. so in our previous example we had 3 mux2 components (i.e. 3 ICs on the breadboard).
- Since port mapping is physical insertion of hardware **it can't be made in a condition** (i.e. `x <= mux2 port map(...)` when `A='0'` ; is totally **incorrect**)
- Unlike software , VHDL statement are **concurrent** , they all execute in the same time not after each other (unless in certain cases to be mentioned later)

OBJECTIVES

- Define VHDL and its usage
- Understand different modeling techniques in designing digital circuits (Dataflow , structural)
- Understand the Hardware created from the VHDL code
- Understand Concurrent statement
- Reuse previously created entity (component instantiation a.k.a port mapping)
- Practice designing with VHDL



TIPS

1. Always Save & Compile before simulation.
2. Read the Error/Warning messages in “Transcript” tap.
3. Change the “Radix” to make the simulation easier (right click on signal name in simulation).
4. Re-writing your code all over again will **NOT** solve your problems.
5. For any Error, check the few lines before the line with error message.
6. Always use Do files instead of Changing the inputs every time.



DEMO#1

- Create Project
- Add files to project (and.vhd)
- Compile (Fix Errors)
- Simulate (force, clock, do)